

Powering and Dimming High-Brightness LEDs with the LM3405 Constant-Current Buck Regulator

National Semiconductor
Application Note 1644
Vinit Jayaraj
January 17, 2008



The LM3405 is a 1A, constant-current buck regulator designed to provide a simple, highly-efficient solution for powering LEDs with the highest power density. The low-feedback reference voltage of 205 mV (typical) allows the use of LEDs with large forward voltages. The LM3405 LED driver comes with an integrated 1A high-side power switch, internal current limit, over-voltage protection and thermal shutdown. The LM3405 driver utilizes current mode control with internal compensation offering ease-of-use and predictable, high-performance regulation over a wide range of operating conditions. This article describes a few of the many application solutions for the LM3405 LED driver. The LM3405 device is offered in

a 6-pin Thin-SOT (TSOT) package and operates at an internal switching frequency of 1.6 MHz, allowing the use of small-value inductors, thereby saving board space.

Typical Application Circuit

Figure 1 shows the typical application circuit using the LM3405 regulator driving a single LED. The boost voltage can be derived from V_{IN} or V_{OUT} . The BOOST to SW voltage (VBOOST-VSW) should never exceed the operating limit of 5.5V, and must be greater than 2.5V for optimum efficiency.

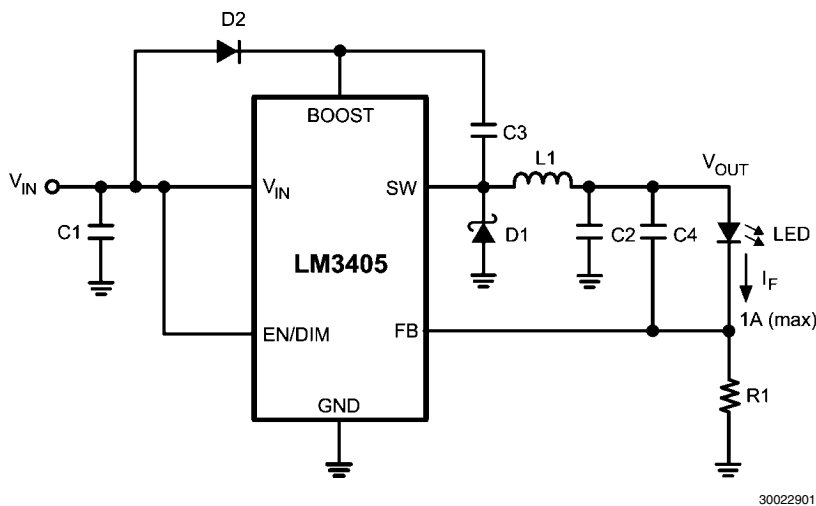


FIGURE 1. Typical Application Circuit

In the above circuit, the maximum V_{IN} is 5V and therefore the boost voltage is derived from V_{IN} . The LM3405 data sheet provides a detailed description of various circuits for boost-voltage generation. The LM3405 driver tightly regulates the FB-pin voltage to 205 mV (typical) and this allows the LED current (I_F) to be set by the following equation:


$$I_F = \frac{205 \text{ mV}}{R1}$$

$R1$ (min) is 200 m Ω such that I_F (max) is limited to 1A. In case of an over current, the internal current limit will trigger and turn

off the internal power switch on a cycle-by-cycle basis. In case of an over voltage (sensed at the FB pin), the internal power switch is turned off. The LM3405 regulator also has a built-in thermal shutdown (with hysteresis) which also turns off the internal power switch if the die temperature exceeds a typical value of 165°C.

PWM Dimming Using the EN/DIM Pin

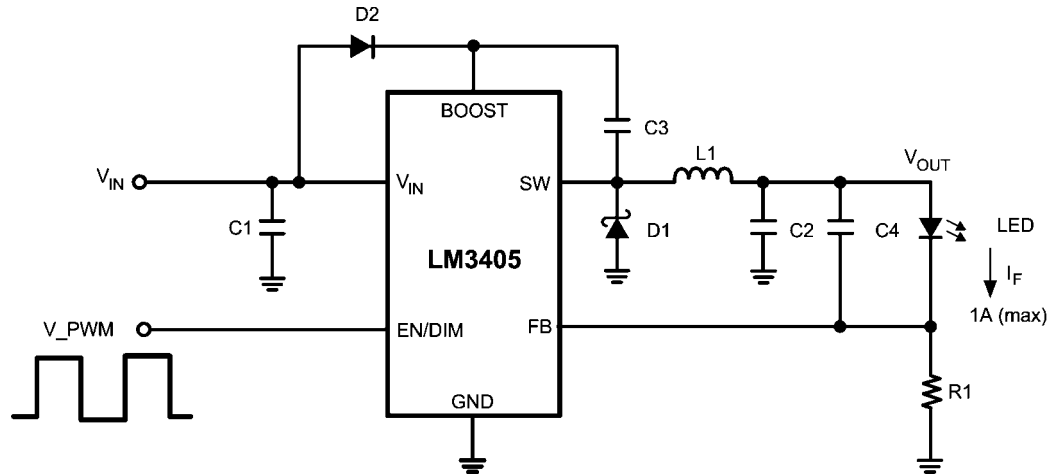The LEDs can be dimmed by applying a PWM-logic signal to the EN/DIM pin of the LM3405 driver as shown in Figure 2.




30022903

FIGURE 2. PWM Dimming of LEDs by Applying a PWM Signal to the EN/DIM Pin

A logic high at V_PWM enables the IC, and a logic low disables the IC. In this manner, the LED current is turned on and off. In order to eliminate flicker, the lowest PWM-dimming frequency is normally chosen to be above 100 Hz. The upper end of the PWM frequency is determined by the turn-on delay of the LM3405. If the V_PWM signal has an ON-time of T_{ON} and a period of T_{PER} , the average I_F is given approximately by the equation below. Note that the delay in enabling and disabling the IC is not included in the following equation. Typically the time delay from the instant where EN/DIM=1 to the instant where I_F is fully established is approximately 100 μ s (see Figure 4).

$$I_{F(average)} = \frac{205 \text{ mV}}{R1} \times \left[\frac{T_{ON}}{T_{PER}} \right]$$

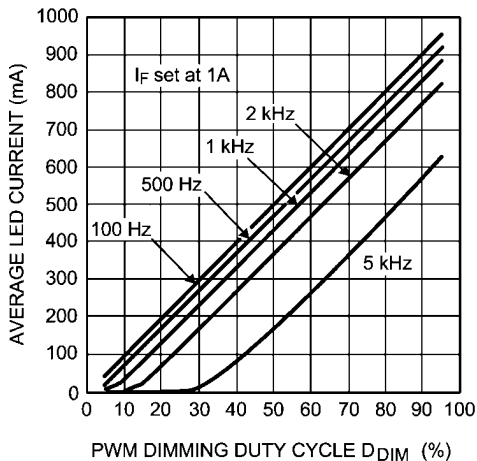
The average LED current is therefore controlled by T_{ON} , T_{PER} , or both and is perceived by the eye as a brightness change. Figure 3 shows the measured average LED current for varying duty cycles and frequencies.



30022905

FIGURE 3. Average LED Current versus Duty Cycle and Frequency of V_PWM at the EN/DIM Pin

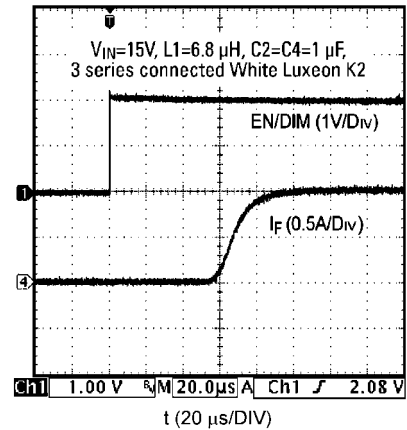The startup delay of the LM3405 device is shown in Figure 4 for an LED-current setting of 1A. This is the delay from the instant when EN/DIM=1 to the instant when I_F settles to 900 mA (90% of the set LED current).




30022906

FIGURE 4. Startup Response of the LM3405 to an EN/DIM Signal with I_F Set at 1A

Deriving a Self-Biased Boost Voltage When Driving Two or More LEDs in Series

In a typical application where two or more LEDs are driven in a single string, the boost voltage is derived from a separate, external low-voltage source so as to meet the (VBOOST-VSW) voltage requirement. This is because when powering two or more LEDs in series, V_{IN} will be greater than 5V and therefore V_{IN} cannot be used to provide VBOOST. In this case, V_{OUT} will also be high and cannot be used to derive VBOOST.

Figure 5 shows another approach for deriving a self-biased boost voltage from the LED string itself without the need for generating a separate low-voltage supply.

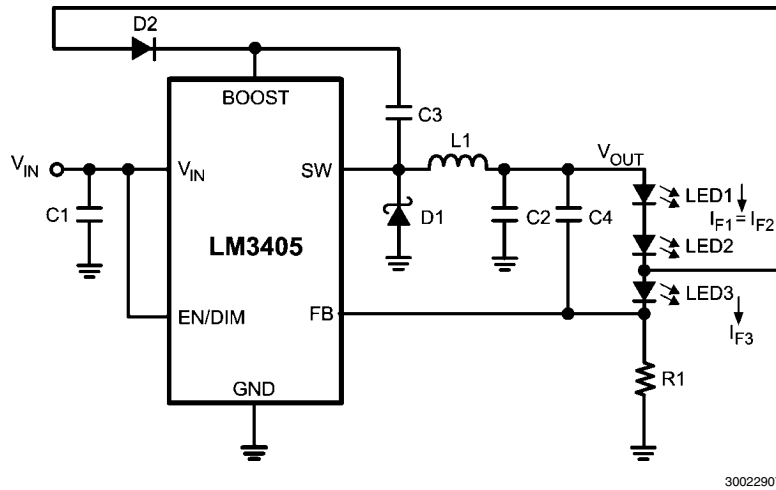

30022907

FIGURE 5. Deriving a Self-Biased Boost Voltage from the LED String When Driving Two or More LEDs in Series

The anode of the boost diode D2 is connected to the anode of LED3. The voltage at the anode of LED3 is approximately equal to 205 mV plus the forward voltage V_F of LED3. This voltage is approximately in the range of 3V to 4V (depending on the I_{F3} current setting) and meets the BOOST to SW voltage requirement. It must be noted that the current through LED1 and LED2 will be slightly larger than the current in LED3 due to the fact that the average charging current for the boost capacitor C3 will now be provided through LED1 and LED2. Therefore, the LED currents are:


$$I_{F3} = \left[\frac{205 \text{ mV}}{R1} \right]$$

$$I_{F1} = I_{F2} = I_{F3} + \overline{I_{C3}}$$

where I_{F1} , I_{F2} , and I_{F3} are the currents in LED1, LED2, and LED3, respectively and $\overline{I_{C3}}$ is the average current charging C3 over one switching cycle. This approach can be used if exact current matching (and hence brightness) is not required between I_{F1} and I_{F3} or between I_{F2} and I_{F3} .

Driving Multiple LED Strings with the LM3405 LED Driver

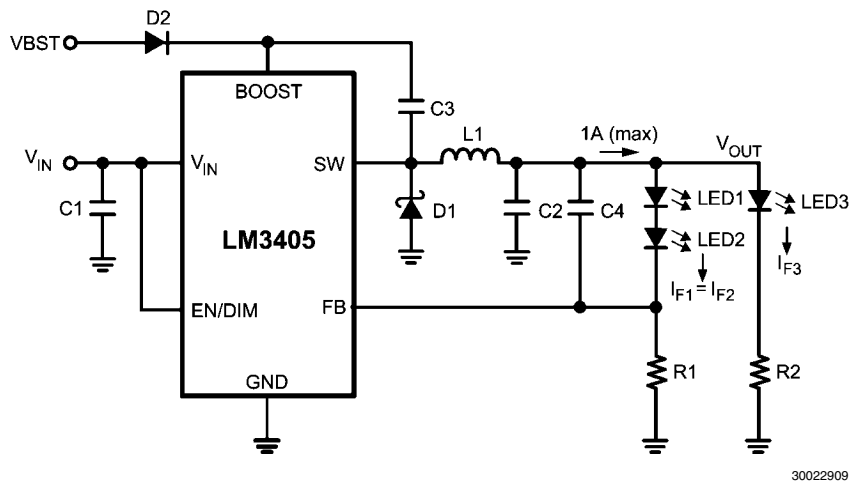The LM3405 LED driver can be used to drive multiple LED strings in parallel as shown in Figure 6. The current in the primary branch (with LED1 and LED2) will be tightly regulated by the feedback loop.



30022909

FIGURE 6. Driving Multiple LED Strings

The current in the secondary branch (with LED3) will be regulated based on V_{OUT} , forward voltage of LED3, and R2. The value of R2 can be adjusted to get the desired brightness for LED3.

$$I_{F1} = I_{F2} = \left[\frac{205 \text{ mV}}{R1} \right] = I_{\text{PRIMARY}}$$

$$I_{F3} = \frac{205 \text{ mV} + V_{F1} + V_{F2} - V_{F3}}{R2} = I_{\text{SECONDARY}}$$

where V_{F1} and V_{F2} are the respective forward voltages of LED1 and LED2 at the primary current level, and V_{F3} is the forward voltage of LED3 at the secondary current level. I_{F1} , I_{F2} , and I_{F3} are the currents in LED1, LED2, and LED3, respectively.

In *Figure 6*, VBST can be connected to an external DC source of 3V to 5V. VBST can also be derived from the cathode of LED3.


If VBST is derived from the cathode of LED3, this VBST can be written as (assuming $V_{F1}=V_{F2}=V_{F3}=V_F=3.8\text{V}$):

$$\text{VBST} = 205 \text{ mV} + V_{F1} + V_{F2} - V_{F3} \approx 205 \text{ mV} + V_F \approx 4\text{V}$$

Note that the average current through LED3 will now be higher since the average current to charge C3 is supplied through LED3 as discussed in the previous section.

Driving Parallel LEDs with the LM3405 LED Driver

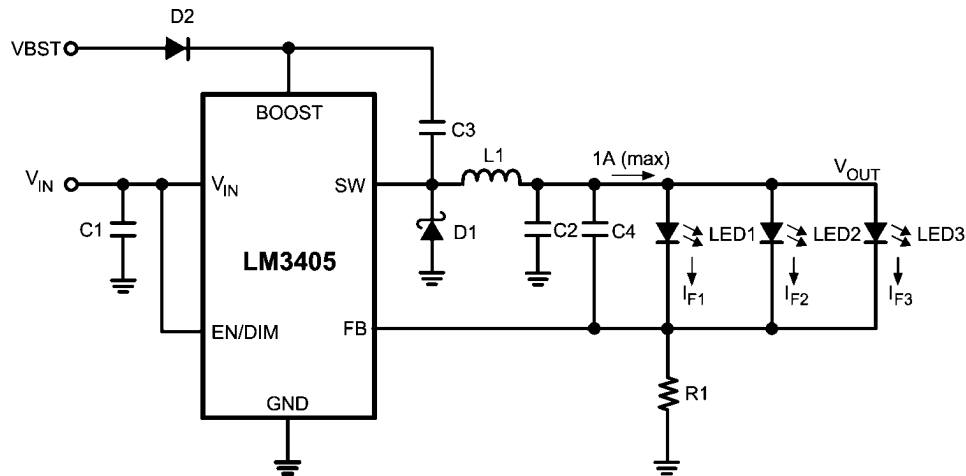Multiple LEDs can be paralleled and connected between V_{OUT} and FB as shown in *Figure 7*.



30022911

FIGURE 7. Driving Multiple LEDs in Parallel

The voltage at the FB pin is regulated to 205 mV by the control loop and therefore the current in R1 is fixed. V_{OUT} is determined by the LED with the highest forward voltage. This solution has the advantage of having a single resistor set the total currents in the LEDs but has no control of equal current sharing between the LEDs.

Conclusion

This article describes a few application solutions using the LM3405 buck regulator. These solutions provide the user with

highly-compact, driving and dimming solutions for high-brightness LEDs. The LM3405 data sheet may be referred to for a detailed description of operation and component design guidelines.

Notes

AN-1644

Notes

For more National Semiconductor product information and proven design tools, visit the following Web sites at:

Products		Design Support	
Amplifiers	www.national.com/amplifiers	WEBENCH	www.national.com/webench
Audio	www.national.com/audio	Analog University	www.national.com/AU
Clock Conditioners	www.national.com/timing	App Notes	www.national.com/appnotes
Data Converters	www.national.com/adc	Distributors	www.national.com/contacts
Displays	www.national.com/displays	Green Compliance	www.national.com/quality/green
Ethernet	www.national.com/ethernet	Packaging	www.national.com/packaging
Interface	www.national.com/interface	Quality and Reliability	www.national.com/quality
LVDS	www.national.com/lvds	Reference Designs	www.national.com/refdesigns
Power Management	www.national.com/power	Feedback	www.national.com/feedback
Switching Regulators	www.national.com/switchers		
LDOs	www.national.com/lido		
LED Lighting	www.national.com/led		
PowerWise	www.national.com/powerwise		
Serial Digital Interface (SDI)	www.national.com/sdi		
Temperature Sensors	www.national.com/tempsensors		
Wireless (PLL/VCO)	www.national.com/wireless		

THE CONTENTS OF THIS DOCUMENT ARE PROVIDED IN CONNECTION WITH NATIONAL SEMICONDUCTOR CORPORATION ("NATIONAL") PRODUCTS. NATIONAL MAKES NO REPRESENTATIONS OR WARRANTIES WITH RESPECT TO THE ACCURACY OR COMPLETENESS OF THE CONTENTS OF THIS PUBLICATION AND RESERVES THE RIGHT TO MAKE CHANGES TO SPECIFICATIONS AND PRODUCT DESCRIPTIONS AT ANY TIME WITHOUT NOTICE. NO LICENSE, WHETHER EXPRESS, IMPLIED, ARISING BY ESTOPPEL OR OTHERWISE, TO ANY INTELLECTUAL PROPERTY RIGHTS IS GRANTED BY THIS DOCUMENT.

TESTING AND OTHER QUALITY CONTROLS ARE USED TO THE EXTENT NATIONAL DEEMS NECESSARY TO SUPPORT NATIONAL'S PRODUCT WARRANTY. EXCEPT WHERE MANDATED BY GOVERNMENT REQUIREMENTS, TESTING OF ALL PARAMETERS OF EACH PRODUCT IS NOT NECESSARILY PERFORMED. NATIONAL ASSUMES NO LIABILITY FOR APPLICATIONS ASSISTANCE OR BUYER PRODUCT DESIGN. BUYERS ARE RESPONSIBLE FOR THEIR PRODUCTS AND APPLICATIONS USING NATIONAL COMPONENTS. PRIOR TO USING OR DISTRIBUTING ANY PRODUCTS THAT INCLUDE NATIONAL COMPONENTS, BUYERS SHOULD PROVIDE ADEQUATE DESIGN, TESTING AND OPERATING SAFEGUARDS.

EXCEPT AS PROVIDED IN NATIONAL'S TERMS AND CONDITIONS OF SALE FOR SUCH PRODUCTS, NATIONAL ASSUMES NO LIABILITY WHATSOEVER, AND NATIONAL DISCLAIMS ANY EXPRESS OR IMPLIED WARRANTY RELATING TO THE SALE AND/OR USE OF NATIONAL PRODUCTS INCLUDING LIABILITY OR WARRANTIES RELATING TO FITNESS FOR A PARTICULAR PURPOSE, MERCHANTABILITY, OR INFRINGEMENT OF ANY PATENT, COPYRIGHT OR OTHER INTELLECTUAL PROPERTY RIGHT.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS PRIOR WRITTEN APPROVAL OF THE CHIEF EXECUTIVE OFFICER AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

Life support devices or systems are devices which (a) are intended for surgical implant into the body, or (b) support or sustain life and whose failure to perform when properly used in accordance with instructions for use provided in the labeling can be reasonably expected to result in a significant injury to the user. A critical component is any component in a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system or to affect its safety or effectiveness.

National Semiconductor and the National Semiconductor logo are registered trademarks of National Semiconductor Corporation. All other brand or product names may be trademarks or registered trademarks of their respective holders.

Copyright© 2008 National Semiconductor Corporation

For the most current product information visit us at www.national.com



**National Semiconductor
Americas Technical
Support Center**
Email:
new.feedback@nsc.com
Tel: 1-800-272-9959

**National Semiconductor Europe
Technical Support Center**
Email: europe.support@nsc.com
German Tel: +49 (0) 180 5010 771
English Tel: +44 (0) 870 850 4288

**National Semiconductor Asia
Pacific Technical Support Center**
Email: ap.support@nsc.com

**National Semiconductor Japan
Technical Support Center**
Email: jpn.feedback@nsc.com